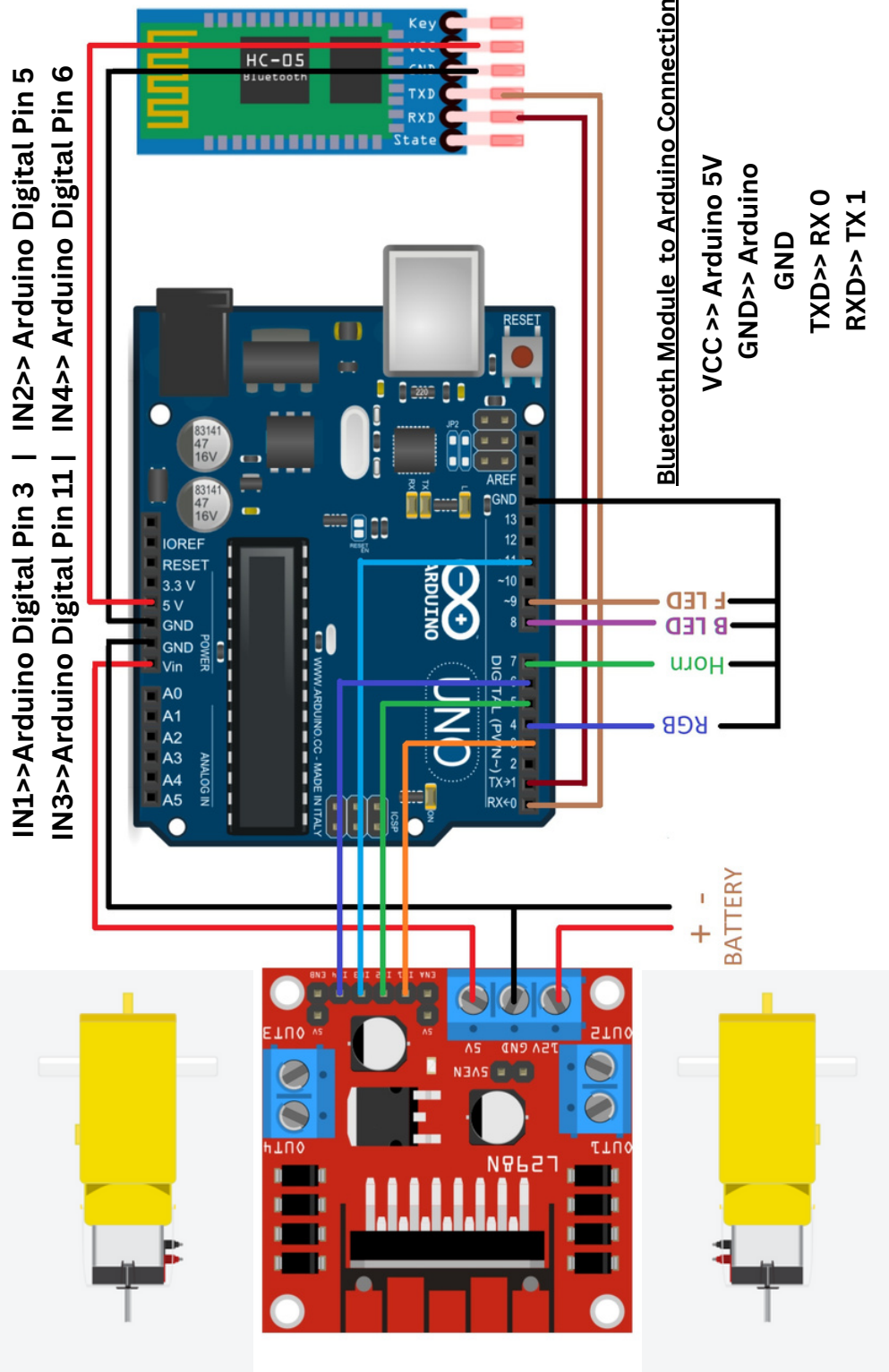


Motor Driver to Arduino Connection

IN1>>Arduino Digital Pin 3 | IN2>> Arduino Digital Pin 5
IN3>>Arduino Digital Pin 11 | IN4>> Arduino Digital Pin 6

Bluetooth Module to Arduino Connection


VCC >> Arduino 5V
GND >> Arduino
GND
TXD >> RX 0
RXD >> TX 1




Component's Name




Bluetooth Module

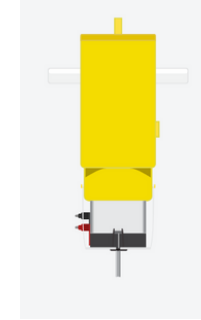

BO Motor

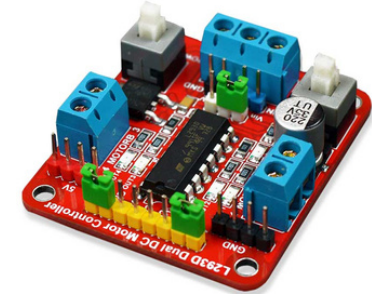

Motor Driver

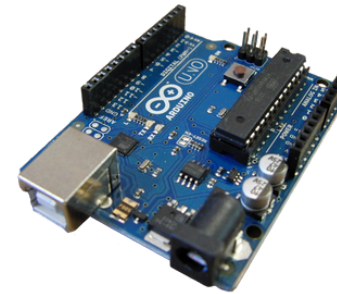

Arduino UNO R3



Jumper Wire

Instructions

Each pin name is given at the front/back of the board. For example: VCC, GND, TXD, RXD of the Bluetooth Module are given at the back of the board.

NB. An app called "Bluetooth RC" is required to control this RC car.

link: <https://bluetooth-rc-car.en.softonic.com/android>

How to pair?

Setting Button >> Connect to Car >> Select HC-05

Done ✓

Redesigned by Plabon Rahman